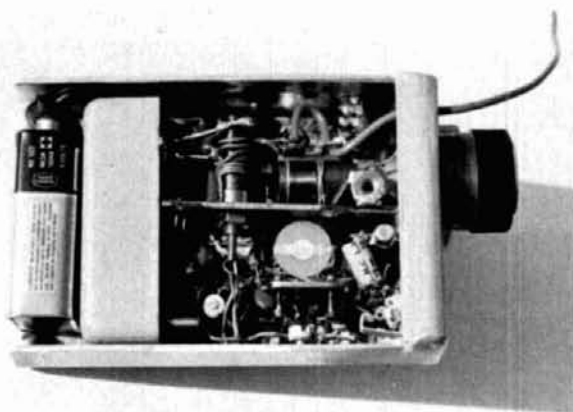


14-MHz superhet uses  
inexpensive ICs



## build a pocket-portable SSB receiver

This article describes the design and construction of a very small, portable 20-meter single sideband receiver. Because some of the more demanding performance requirements can be relaxed in favor of small size and reduced component count, the project also represents an interesting design exercise in value engineering.

For example, reference 1 states that performance limitations are the principal drawbacks of integrated circuit mixers. Yet for a portable receiver in use in a remote location — say on a camping trip — small size

and high gain may be more important than strong signal performance. Reduced complexity is also attractive to inexperienced builders; using ICs simplifies the design, since they can be considered as building blocks already designed by the manufacturer's specification sheets. The only real work, then, is selecting the best ICs and connecting them together.

### circuit description

Figure 1 shows that the receiver is a conventional single conversion superheterodyne design with a 9-MHz i-f. Major circuit blocks are represented by IC part numbers with the exception of the AGC. The following circuit theory of operation is presented in a sequence beginning at the output and proceeding toward the input, which is the recommended sequence for construction. Dividing a large project into several small tasks makes the work seem easier, and the completed output stages can be used as a test aid to align and troubleshoot preceding stages assembled later.

### audio amplifier

Figure 2 shows the National Semiconductor LM386 Low-Voltage Audio Power Amplifier, which is used to drive an earphone. The main advantage of this component is low battery drain and operation from a 9-volt

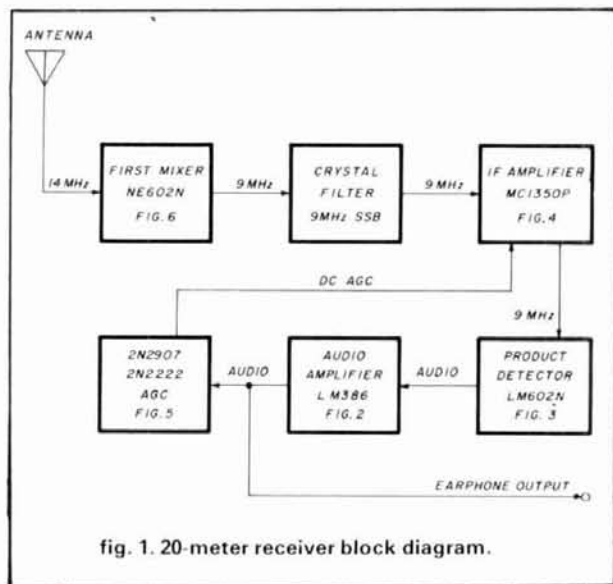


fig. 1. 20-meter receiver block diagram.

Cliff Klinert, WB6BIH, 1126 Division Street, National City, California 92050

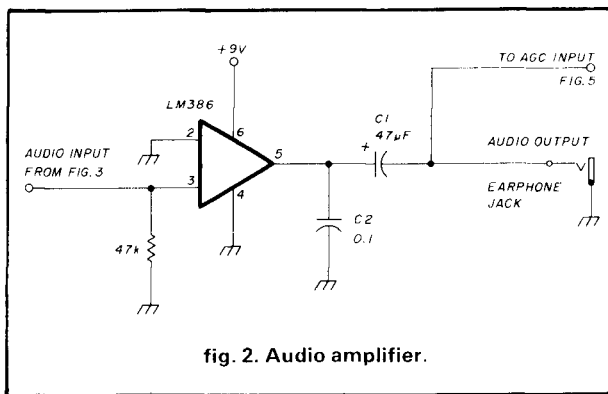


fig. 2. Audio amplifier.

battery. The 9-volt power source was considered essential for convenience in obtaining batteries while traveling.

Peripheral components increase circuit complexity, but provide an opportunity to shape the receiver audio frequency response. Signal frequencies below a few hundred Hz and above a few kHz should be attenuated by selecting audio coupling and bypass capacitor values carefully. Each capacitor (and associated resistance) provides a 6-dB per octave roll-off beyond the break point. The half-power break frequency is:

$$F = \frac{0.159}{RC}$$

where  $F$  is in Hz,  $R$  is in ohms, and  $C$  is in farads. For example, the output coupling capacitor,  $C1$  of **fig. 2**, gives a low-frequency rolloff frequency calculated as 160 Hz. This is assuming that the LM386 output impedance is very low and the earphone offers the principal resistance in the circuit. I actually measured the earphone impedance to be 21 ohms at 1000 Hz when the calculations gave confusing results. The earphone is presumably 16 ohms, but it could have been 8 ohms. The following data was taken for selected capacitors using one-half voltage for the measurement point, which resulted in slightly lower frequencies (6 dB down):

330 $\mu$ F	10 Hz
100 $\mu$ F	70 Hz
47 $\mu$ F	120 Hz

These results suggest that it may be better to substitute capacitors and sweep the frequencies with an audio oscillator than perform calculations when circuit resistance may be inconvenient to determine. In fact, components were selected experimentally, but the equation is helpful for awareness of circuit operation and to provide a starting point. A bypass capacitor (0.047  $\mu$ F) in the product detector output provides a similar function for high frequencies, and the equation is the same.

$C2$ , added to cure a high-frequency oscillation, may

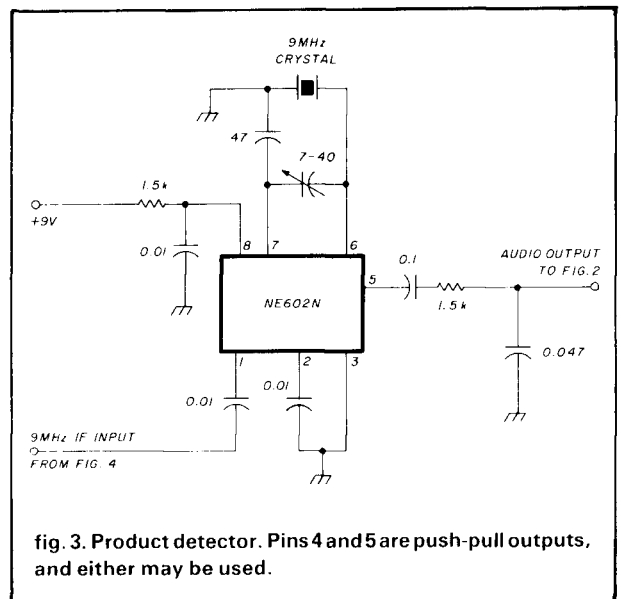


fig. 3. Product detector. Pins 4 and 5 are push-pull outputs, and either may be used.

not be necessary in all cases. A large capacitor bypassing the audio power amplifier wastes power and may cause instability.

Tests showed that a 30-millivolt, 1000-Hz input signal provided a 600-millivolt output for a gain of 20. Current drain was 5 milliamperes at 9 volts.

### product detector

The Signetics NE602 shown in **fig. 3** is used for the product detector as well as the first mixer. One of the more popular Gilbert Cell mixers, it also contains a voltage regulator and bias, an oscillator, and an rf amplifier. These features are implemented with an absolute minimum of external components. Pin 7, the oscillator emitter, can be used as a test point for checking oscillator operation. 350 millivolts of 9-MHz sine wave signal is a typical value. The capacitors connected to pin 7 must be adjusted for the correct operating carrier frequency to match the crystal filter. Power voltage for the NE602 is 6 volts, which is supplied to pin 8 through the 1.5k resistor. Application of a 400-microvolt 9-MHz i-f input signal to pin 1 gives a 150-millivolt peak-to-peak earphone output when connected to the audio amplifier **see fig. 2**. The current drain is an economical 2.5 milliamperes. More information on the NE602 is provided in the first mixer circuit description.

The resistor/capacitor network connected to pin 5 shapes the audio frequency response as described in the previous section. The 0.1  $\mu$ F capacitor provides low frequency rolloff to complement  $C1$  of **fig. 1**. The 0.047  $\mu$ F capacitor bypasses high frequencies.

### i-f amplifier

A Motorola MC1350P television i-f amplifier was

used for the 9-MHz i-f amplifier **fig. 4**. This popular IC features high gain, excellent stability, and a very handy AGC input terminal. The MC1350P was intended for a 12-volt power supply, but works well on 9 volts with a current drain measured at 12 milliamperes. No particular effort was expended to wind T1 with a 14-turn primary (center tapped) and a 14-turn secondary on an FT 37-61 ferrite toroid core with No. 27 AWG wire. It seemed to resonate with about 15 pF of capacitance provided by a 9- to 20-pF variable, but it also works without the capacitor. Be sure to ground the AGC input, pin 5, for maximum gain while testing. Performance testing now shows that only 0.7 microvolts RMS 9-MHz input is required to produce a 100-millivolt peak-to-peak earphone audio output. The MC1350 gain was 50 dB with a 200 microvolt i-f output for the 0.7 microvolt input. Total receiver current drain at this point was 20 milliamperes.

### crystal filter


The crystal filter is the largest and potentially most expensive item. The price of a new crystal filter would make it impractical for so simple a project. I first considered the crystal filter as an optional or less critical item, but the obvious performance improvement made it a necessity. The filter and BFO crystal can be a junk box or surplus item. The 9-MHz filter used for this project was purchased for about \$20 from a *ham radio* advertiser a few years ago, but swap meets and hamfests are also good sources. Be sure to get a BFO crystal with the filter, but if several filters are available inexpensively it may be better to break apart a filter to get an oscillator crystal. With luck it may be possible to tune the BFO to the right frequency with the oscillator capacitors and avoid the expense of ordering a crystal. At this point, a substantial effort may be required to sweep the filter with a signal generator while monitoring the receiver audio output and adjusting the BFO frequency for the desired frequency response.

### automatic gain control


AGC is a truly optional feature that could be substituted with a potentiometer voltage divider connected to the MC1350 AGC input. Some experience using this method showed that the "two-knob" tuning method required was somewhat inconvenient considering the small controls and lack of panel space. Also, eliminating the manual gain control provided additional space for an AGC circuit.

The AGC characteristics of the MC1350 used were measured and tabulated as follows:


Pin 5 voltage	4.50 volts max gain
	4.77 volts min gain

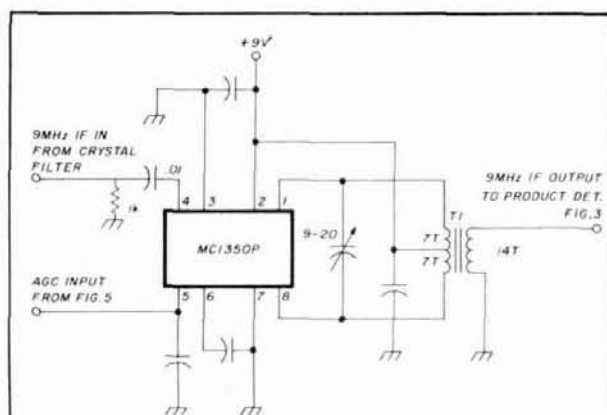

**fig. 4.** I-f amplifier. All capacitors are 0.01 disc except the 9-20 pF variable.

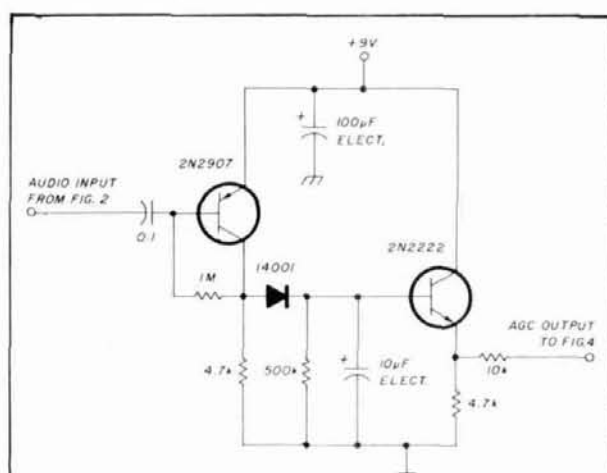

**fig. 5.** Automatic gain control.

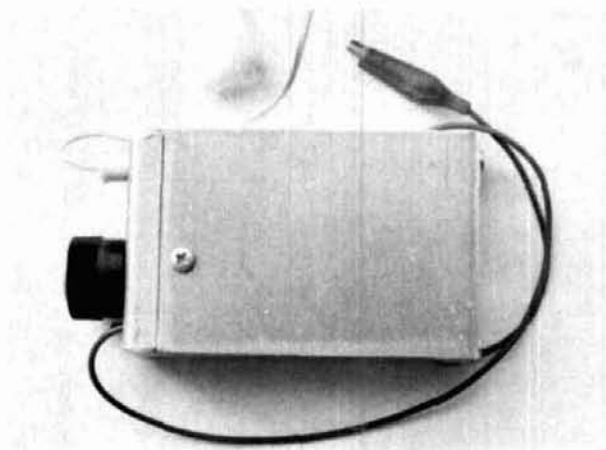

**Photo A.** The receiver is housed in a sheet aluminum enclosure. The aluminum was bent in a brake and the corners were TIG (Tungsten Inert Gas) welded. The clip lead is the antenna connector.



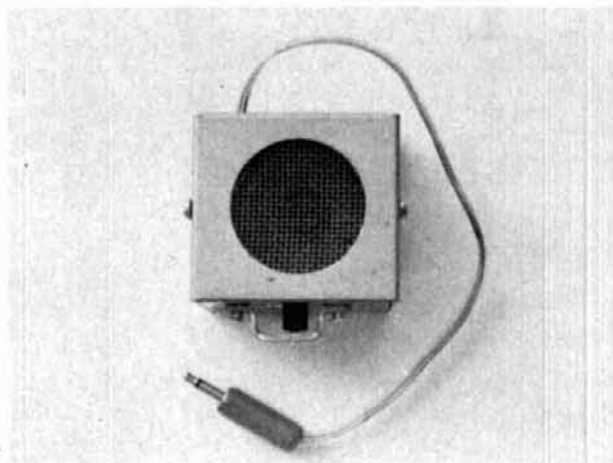


Photo B. This small box contains an amplifier and a speaker. The amplifier is the same as shown in fig. 2. No volume control is required when used with the receiver.

Soldering the components together does pose some problems, however. As can be seen in the photographs, it's very difficult to see some of the components. Repairs seem impossible. Don't solder to the crystal can near any of its solder seals; doing so may cause a vacuum leak, spraying molten solder on the quartz.

The electronic aspects of construction require use of an oscilloscope with a high impedance (x10) probe, an audio oscillator, and an rf signal generator. A frequency counter is handy but not essential. The x10 probe allows monitoring the oscillators with a minimal amount of frequency shift due to loading by the probe. I connect my frequency counter to the oscilloscope channel 1 output for checking the oscillator frequency. This is especially handy for setting up the BFO when the exact frequency is known, but the BFO frequency is subject to adjustment later "by ear" when listening to SSB signals. The first mixer oscillator can be adjusted with a receiver or signal generator, and will also require considerable adjustment to obtain the right frequency range.

### conclusion

This receiver has enough gain to be used with almost any metal object as an antenna. I used a clip lead as an antenna connector. It's handy to carry a convenient length of insulated flexible wire for those times when there's a chance to rig a makeshift antenna in a tree or bush. Twenty meters provides good listening most times of the day or night, with some DX in the early morning.

This article presented a few applications of some simple but versatile integrated circuits. My intent was to present a few circuits that might inspire the reader

to develop new applications. For example, I mounted an LM386 with a battery and speaker in a small box to carry with the receiver. (See Photo B.) Future projects for the NE602 might include a tunable short-wave converter for an a-m car radio, or an aircraft band receiver with an MC1350 i-f amplifier.

### references

1. Gary A. Breed, "Mixers: Making the Right Choice," *rf design*, August, 1986.
2. "Applying the Oscillator of the NE602 in Low-Power Mixer Applications," Signetics Applications Note No. AN1982, October, 1985. (Signetics Corporation, 811 East Arques Avenue, Sunnyvale, California 94088-3409.)

ham radio

## K.V.G. CRYSTAL PRODUCTS



### 9 MHz CRYSTAL FILTERS

MODEL	Application	Bandwidth	Poles	Price
XF-9A	SSB	2.4 kHz	5	\$53.15
XF-9B	SSB	2.4 kHz	8	72.05
XF-9B-01	LSB	2.4 kHz	8	95.90
XF-9B-02	USB	2.4 kHz	8	95.90
XF-9B-10	SSB	2.4 kHz	10	125.65
XF-9C	AM	3.75 kHz	8	77.40
XF-9D	AM	5.0 kHz	8	77.40
XF-9E	FM	12.0 kHz	8	77.40
XF-9M	CW	500 Hz	4	54.10
XF-9NB	CW	500 Hz	8	95.90
XF-9P	CW	250 Hz	8	151.20
XF-910	IF noise	15 kHz	2	17.15

### 10.7 MHz CRYSTAL FILTERS

WRITE FOR FULL DETAILS OF CRYSTALS AND FILTERS  
Export inquiries invited. Shipping: \$3.75

### MICROWAVE MODULES EQUIPMENTS

Use your existing HF or 2M rig on other VHF or UHF bands.

#### RECEIVE CONVERTERS

MMk 1691-137	259.95
MMk 1296-144G	189.95
MMc 439-ATV	94.95
MMc 432-28(S)	59.95
MMc 144-28(HP)	69.95
MMc 144-28	54.95

#### LINEAR TRANSVERTERS

MMI 1296-144G	369.95
MMx 1268-144	289.95
MMI 432-28(S)	289.95
MMI 144-28(R)	349.95
MMI 144-28	189.95
MMI 435-28(S)	299.95

### LINEAR POWER AMPLIFIERS

2M		70cm	
MML 144-30-LS	144.95	MML 432-30-L	189.95
MML 144-50-S	119.95	MML 432-50	229.95
MML 144-100-S	224.95	MML 432-100	439.95
MML 144-100-LS	249.95		
MML 144-200-S	439.95		

### ANTENNAS

2M:		142	
10XY-2M	\$74.95		
70cm:			
70/MBM28	\$44.95	LOOP YAGIS	
70/MBM48	64.95	1268-LY	\$49.95
70/MBM88	94.95	1296-LY	49.95
DY20-900 MHz	79.95	1691-LY	59.95
		order loop yagi connector extra	

Send 66¢ (3 stamps) for full details of all our VHF & UHF equipments and KVG crystal products.

Shipping: FOB Concord, Mass.



# si

(617) 263-2145  
SPECTRUM  
INTERNATIONAL, INC.  
Post Office Box 1084  
Concord, MA 01742, U.S.A.