modulation. If you run about 15 watts the positive peaks will be somewhere around 115% while the negative peaks remain 100%. Works great for driving a grounded grid linear. below no iron required. What's not to like?!? The transmitter output is adjustable from zero to twenty five watts output with 100% Now you can have a nice small 25 watt transmitter/exciter requiring only four tubes and NO modulation transformer. Hi-fi and Line In 300mU 1500V Test Insul 6.30 Filament For 807 10k 8 9 ,300 000 **102**h -75 늦 £33 1.985mHz 中 → 10uF 100 6LF6 ~220pf 첫 100 6AG7 1mH .001uF 500pf ODI checked bu engineer RCS 6LF6 001 200PF / 일 일 4 TURNS AROUND 47 DHM 2W 100 2.5mH 1504 .001uF size code id drawing no SERIES MOD. XMTR **~** ₽ 5 9 9+40 500J O+1100 BOB STOUT (♥) #47 Bulb MB9ECK stout\xmtr.sch sheet