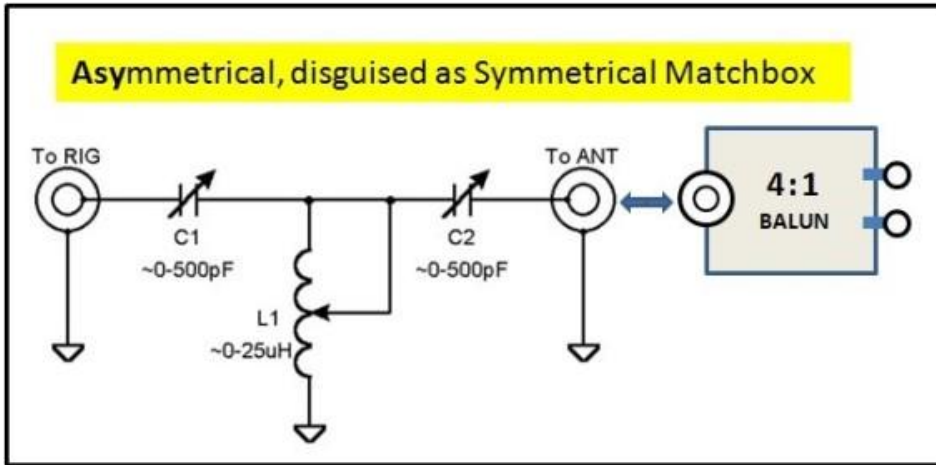


## THE PAPER TIGER:




**THIS IS NOT A SYMMETRICAL MATCHBOX.**

And when running high power you will probably have problems with RF in the shack, especially if the matchbox has a 4:1 balun on the antenna side. **The balun does not properly function as a balun when the SWR is too high.** As a result you will have common mode current in the matchbox and in the shack.

**You may notice this by:**

- Equipment going into "fault"
- Hot mic or hot key, causing RF burns
- TVI, BCI, etc.

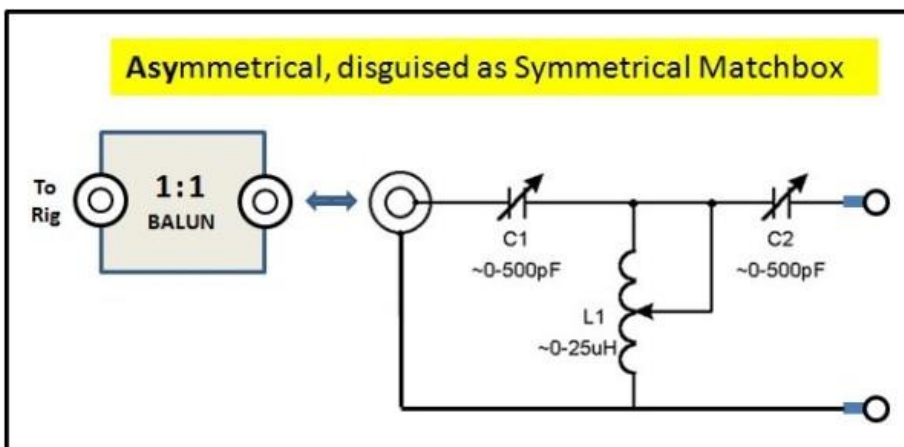**So the next "GURU" said "Do it this way:"**



**OK, this looks better:**

- The enclosure of the Matchbox is now floating above ground; nothing is grounded inside the matchbox.
- The Balun is seeing its design impedance.
- Problem is, in practice it only works just a little bit better than the circuit above.
- In many attempts to perfect this, including trying several different types of baluns, I continued to have problems with RF in the shack when running high power.


- Yet when I replaced this with two different high power [true] symmetrical matchboxes, there were no more problems at all !

**Bottom Line, this is better than the circuit above, but still just a work-around with hitches. If this is the best you can do, go ahead. But there are much better solutions.**

**MORE TECHNICAL DETAIL ON THIS TOPIC, BY W7EL, IS AVAILABLE ON THE FOLLOWING LINKS:**

- <http://eznec.com/misc/ibalbrf.txt>
- <http://eznec.com/misc/ibalun.txt>
- <http://www.eznec.com/Amateur/Articles/Baluns.pdf>

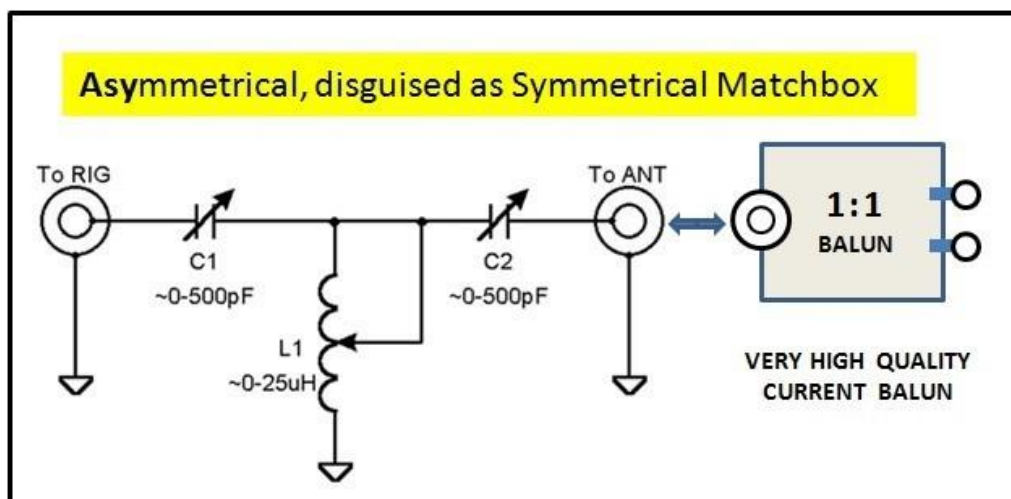**THIRD TIME IS THE CHARM: THIS ONE IS NOT BAD:**



**It's not bad, but it's not great.** However with this circuit I was able to run one kilowatt without burning my fingers on the key, or my lips on the mic. A prerequisite for this is, you have to have a good matchbox which has no problem dealing with the high voltage due to the higher impedance when not using the 4:1 transformation in front of it. The variable capacitors should be rated about 6KV or more.

**In my specific case, I used a Ten-Tec Model 238B, which is a very good L-Network.**

A good T-Network will also work, if the capacitors are of the values shown here and have wide enough plate spacing.

**NOTE: although my Ten-Tec Model 238B has a built-in 4:1 balun, I do not use it for the reasons explained above. Instead I use an external home-brew 1:1 current balun.**

**I have been using this for the past 10 years.**

Recent reports from others confirm my experience.

For more explanation on why a 1:1 balun is better here than a 4:1 balun, see also:

- *"Windom- und Stromsummen-Antennen"* by Karl Hille, DL1VU, ISBN 3-910159-14-1, pages 106 and 107.
- [Tuner Balun Ratios](#) by Steve Hunt, G3TXQ



NEED YOU WORRY ? . . . and . . . HOW DO YOU KNOW ?

**If you are running low power, up to 100w or so,  
you can probably use any of these circuits shown on this page  
without incurring any problem.  
(Even the cheap work-arounds will work.)**

If you have a little problem with RF in the shack, simply insert an RF Choke (beads over coax) in the transmission line between the matchbox and transceiver and your will probably be OK.

**IF YOU ARE RUNNING HIGH POWER (500+w)**

**YES, YOU SHOULD BE CONCERNED.**

**HOW YOU WILL KNOW:**

- You may have RF all over the shack.
- Transceivers or Amplifiers may be randomly going to **FAULT** condition.
- You may have interference with other equipment such as televisions or telephones.
- You will burn your lips on your mic and your fingers on your key.

**IN THIS CASE YOU SHOULD FOLLOW THESE PRIORITIES:**

- Get yourself a good, high power symmetrical matchbox, like a 1KW Annecke Symmetrical Koppler, Johnson Viking Matchbox, MFJ-976, Palstar BT-1500 or AT-2K-BT (BT=Balanced Tuner. It must be the model with "BT", not the previous model).
- If you only need one or two bands, consider home brewing a symmetrical tuner.
- If a symmetrical tuner is not an option at this time, then use the circuit showing a 1:1 current balun on the antenna side of the matchbox.
- Use either of the other two in a pinch, but don't be surprised if you get some **shocking results**. In this case it usually helps to insert an RF-Choke (beads over coax) between the matchbox and the amplifier.